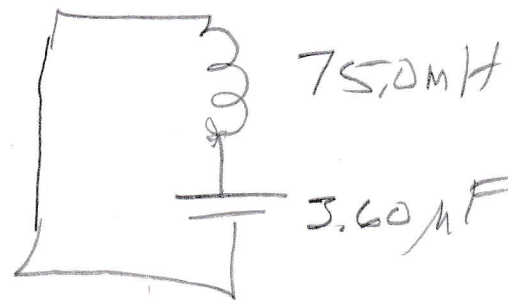


Homework 31.1

An oscillating LC circuit consists of a 75.0 mH inductor and a 3.60 μF capacitor. If the maximum charge on the capacitor is 2.90 μC , what are the (a) total energy in the circuit and (b) the maximum current?

$$U_e = \frac{1}{2} CV^2 = \frac{1}{2} \frac{Q^2}{C}$$

$$\frac{1}{2} \frac{Q^2}{C} = \frac{\frac{1}{2} (2.9 \times 10^{-6})^2}{3.60 \times 10^{-6}}$$



$$c) \quad U = 1.17 \mu\text{J}$$

$$b) \quad U = \frac{1}{2} L I_{\text{max}}^2$$

$$I_{\text{max}} = \sqrt{\frac{2U}{L}} = \sqrt{\frac{2 \times 1.168 \times 10^{-6}}{75 \times 10^{-3}}}$$

$$= \sqrt{.0311 \times 10^{-3}} = \sqrt{0.311 \times 10^{-4}}$$


$$= \sqrt{0.311} \times 10^{-2}$$

$$= 0.558 \times 10^{-2}$$

$$I_{\text{max}} = 5.58 \text{ mA}$$

Homework 31.35

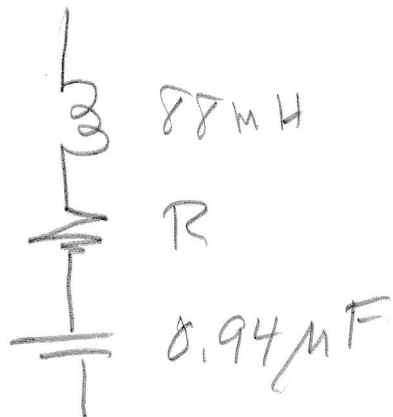A coil of inductance 88 mH and an unknown resistance and a 0.94 μF capacitor are connected in series with an alternating emf of frequency 930 Hz. If the phase constant between the applied voltage and the current is 75° , what is the resistance of the coil



$$\omega = 2\pi \times 930$$

$$\theta = 75^\circ$$

$$= \tan^{-1} \left(\frac{\omega L - \frac{1}{\omega C}}{R} \right)$$

$$\omega L = 2\pi 930 \times 88 \times 10^{-3}$$

$$X_L = \omega L = 514 \, \Omega$$

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi 930 \times 0.94 \times 10^{-6}} = 182 \, \Omega$$

$$\tan 75^\circ = \frac{\omega L - \frac{1}{\omega C}}{R} = 3.73$$

$$R = \frac{332}{3.73} = 89.0 \, \Omega$$

Homework 31.39

Remove the inductor from the circuit in Fig. 31-7 and set $R = 200 \, \Omega$, $C = 15.0 \, \mu\text{F}$, $f_d = 60.0 \, \text{Hz}$, and $\xi_m = 36.0 \, \text{V}$. What are (a) Z , (b) ϕ , and (c) I ? (d) Draw a phasor diagram.


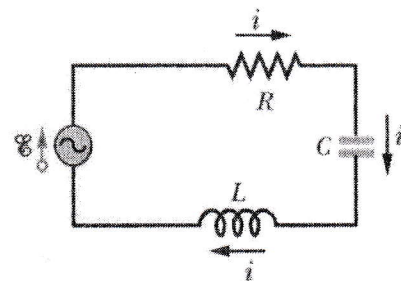


Figure 31-7 A single loop circuit containing, a resistor, a capacitor, and an inductor. A generator, represented by a sine wave in a circle, produces an alternating emf that establishes an alternating current; the direction of the emf and current are indicated here at only one instant.

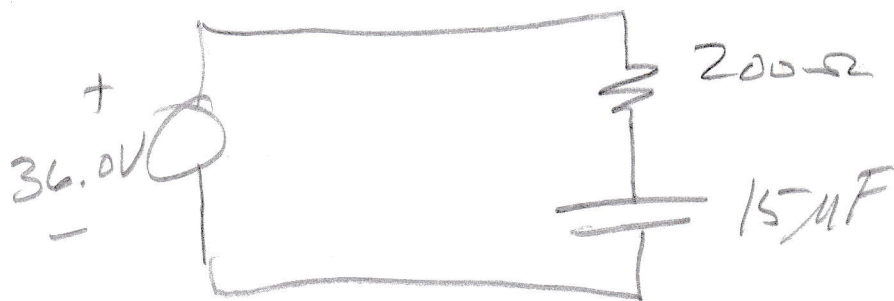

$$X_C = \frac{1}{\omega C} = \frac{10^6}{120\pi \times 15} = 176.8 \, \Omega$$



$$a) \, Z = R - jX_C = 200 - j176.8 \, \Omega$$

$$(a) \, |Z| = \sqrt{(200)^2 + (176.8)^2} = 267 \, \Omega$$

$$(b) \, \phi = \tan^{-1}\left(\frac{-X_C}{R}\right) = \tan^{-1}\left(\frac{-176.8}{200}\right) = -41.5^\circ$$

$$(c) \, V = IZ \quad I = \frac{V}{Z} = \frac{36.0}{267} = 135 \, \text{mA}$$

$$I = \frac{V}{Z} = \frac{36}{267} \angle -41.5^\circ = 135 \, \text{mA} \angle 41.5^\circ$$

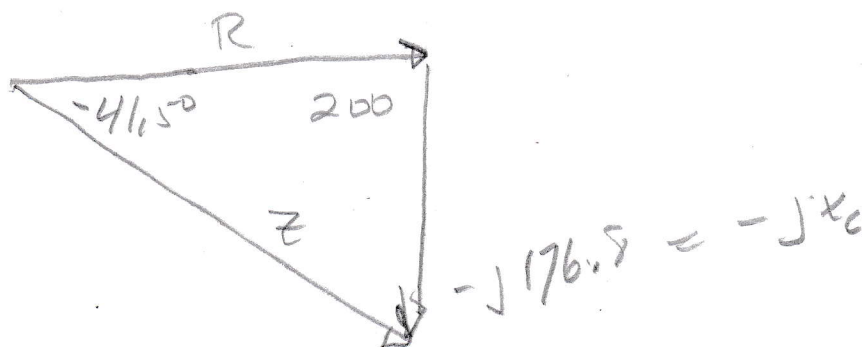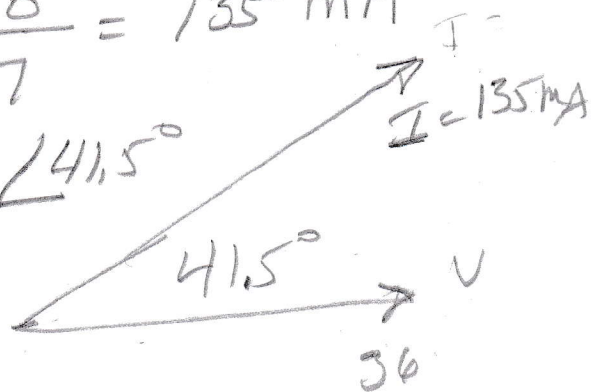

Homework 31.53

An air conditioner connected to a 120 V rms ac line is equivalent to a $12\ \Omega$ resistance and a $1.3\ \Omega$ inductive reactance in series. Calculate (a) the impedance of the air conditioner and (b) the average rate at which energy is supplied to the appliance.

$$a) \quad Z = 12 + j 1.3$$


$$|Z| = \sqrt{12^2 + 1.3^2} = 12.07\ \Omega$$

$$|I| = \frac{V}{|Z|} = \frac{120}{12.07}$$

$$b) \quad P = I^2 R = \left(\frac{120}{12.07} \right)^2 \times 12 = \underline{\underline{1.19\text{ kW}}}$$

Homework 31.63

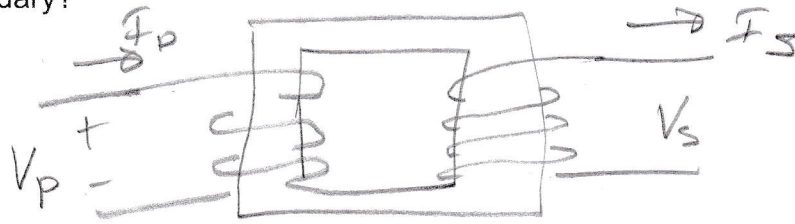A transformer has 500 primary turns and 10 secondary turns. (a) If V_p is 120 V (rms), what is V_s with an open circuit? If the secondary now has a resistive load of $15\ \Omega$, what is the current in the (b) primary and (c) secondary?



$$N_p = 500 \quad N_s = 10$$

$$\frac{V_s}{V_p} = \frac{N_s}{N_p} = \frac{10}{500}$$

$$a) \quad V_s = \frac{V_p}{50} = \frac{120}{50} = 2.4 \text{ Volts}$$

$$\frac{I_s}{I_p} = \frac{500}{10} = 50$$

$$c) \quad I_s = \frac{2.4}{15} = 160 \text{ mA}$$

$$b) \quad I_p = \frac{I_s}{50} = \frac{160}{50} = 3.2 \text{ mA}$$